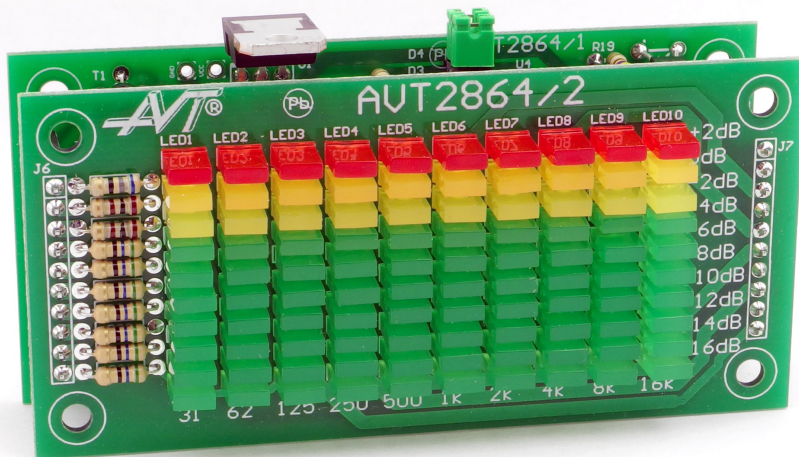




AVT 2864



ASSEMBLY DIFFICULTY



Circuit for analysing and displaying the spectrum of an audio signal, very often used (and found) in the audio paths of so-called high-end audiophile equipment. In addition to the analogue part, the kit uses digital signal processing, or DSP. The 'heart' of the analyser is the ATmega8 processor. The A/D converter contained in its structure serves to convert the analogue signal into a digital signal accordingly, and this is routed to a display realised from an array of LEDs.

The filters used to light up relevant 'bars' are provided in the software. This has greatly simplified the design of the analyser, so that even an intermediate electronics technician can build and use this device.

The set is based on the design with the same title published in Electronics for All 05/2008. Full version of the original manual is available to download here: <https://bit.ly/3opZDPH>



Characteristics

- monophonic spectrum analyser - 1 channel
- signal spectrum presented on a 10-bar display
- filter mid frequencies: 31 Hz, 62 Hz, 125 Hz, 250 Hz, 500 Hz, 1 kHz, 2 kHz, 4 kHz, 8 kHz and 16 kHz
- signal amplitudes that light up subsequent LEDs in the bar: -16 dB to +2 dB in 2 dB steps
- 0 dB indication corresponds to an input signal with an amplitude of 0.2 V
- operation in bar or point display mode
- maximum amplitude display mode
- spectrum presentation on the field from multicoloured LEDs (100 pcs)
- power supply: 9-12 VDC
- board sizes:
LED board 96×45 mm, main board 96×45 mm

Circuit description

Circuit diagram of the main board is shown in Figure 1, and the display diagram in Figure 2. The supply voltage of 9-12 V is fed to the VCC and GND points. It is filtered through capacitors C1 and C2 and goes to stabiliser U1. Voltage from stabiliser output, blocked with capacitors C3 and C4, powers the microcontroller U3, and the LED display. The audio signal goes to IN

point and via capacitor C9 enters the non-inverting input of operational amplifier U2. Resistors R34, R35, R36, R37 and diodes D1, D2 form a amplifier supply voltage limiter U2. Resistors R36 and R37 form a voltage divider that pre-polarises the ADC input with approximately 2.5V. Amplified audio signal from the output of operational amplifier U2 is via the capacitor

Because the Almega8 chip has too few legs to directly handle a display of 10 columns and 10 rows, receive analogue audio data and read the status of jumpers J4

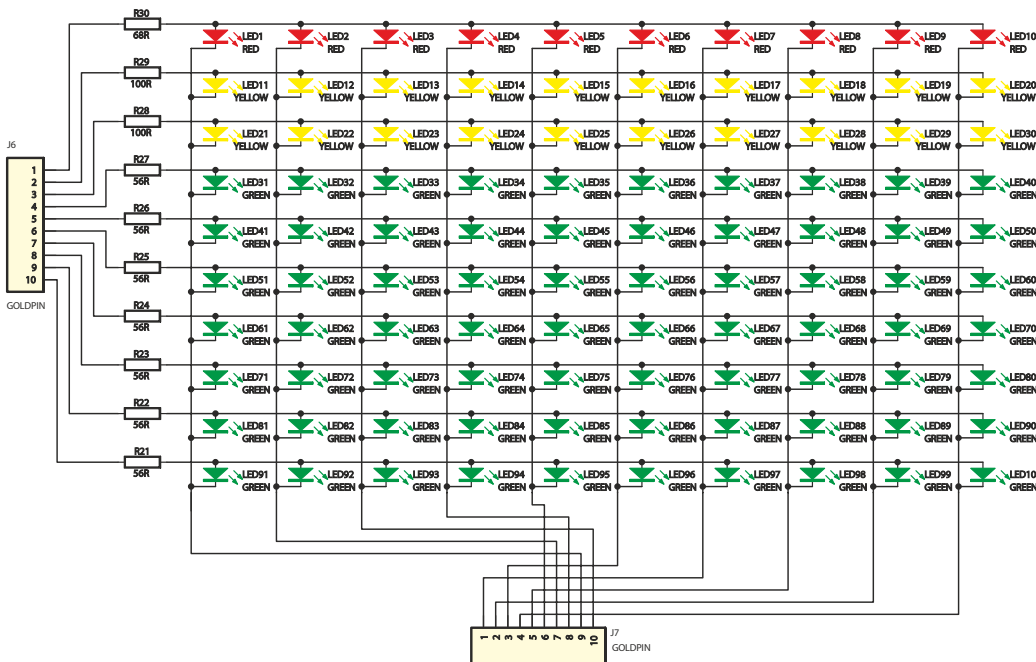


Fig. 2. Schematic diagram of the display

and after they are inserted into the holes in the boards. Mount the transistors T1...T20 possibly close to the board. Mount the stabiliser U1 as shown in the photos. Such mounting will enable easy screwing on the heatsink. Just a few more sentences about the diodes LED1... LED100. In order to install them in a relatively simple manner you have to use a well-known trick. It involves inserting the legs of the diodes into the appropriate holes, turning the board upside down (diodes down, soldering points up) and positioning so inverted plate on some flat surface, for example, on a table (of course, when turning protect the diodes from falling out, as a piece of paper that you take out once the board is laid). In this way, the diodes will be in constant distance from the board. Now, solder one leg

of each diode at a time. It is best to shorten at once the legs that are soldered first, to make easier soldering of further legs. After soldering all legs needed, turn the board over and set the diodes straight, because they will certainly be a little twisted and tilted. Once you have this done, you can solder the "second" legs of each diode. Once assembled, the circuit will not require any start-up procedure and should immediately work correctly. The analyser should be controlled during normal operation by an audio signal with an amplitude of up to approximately 0.2 Vpp. Insert or not jumpers J3 and J4 to activate the corresponding operating mode.

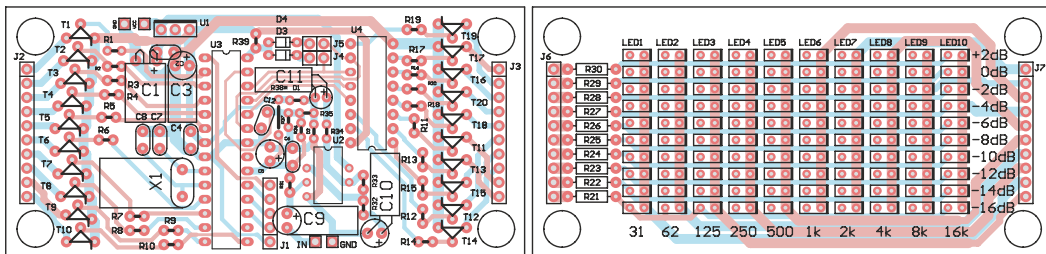


Fig. 3. Arrangement of components on the PCBs

List of components

MAIN BOARD:

Resistors:

R1-R10, R34:	4.7 kΩ
R11-R20:	470 Ω
R31, R33:	68 kΩ
R32, R35:	6.8 kΩ
R36, R37:	47 kΩ
R38:	(do not mount)
R39:	10 kΩ

Capacitors:


C1:	220 uF / 16 V
C2, C4, C6:	100 nF ceramic
C3:	22 uF
C5:	100 uF
C7, C8:	18 pF
C9, C11:	4.7 uF
C10:	10 uF
C12:	4.7 nF ceramic

Semiconductors:

D1-D4:	1N4148
T1-T10:	BC557
T11-T20:	BC337
U1:	7805
U2:	TL071
U3:	ATmega8
U4:	4028

Other:

Q1:	quartz 18 MHz
J1:	goldpin strip 1×5
J2, J3:	goldpin socket 1×10
J4 and J5:	goldpin angle strip 2×2 + jumpers

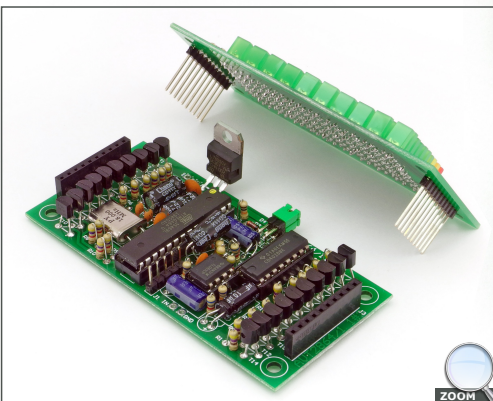

DISPLAY:

Resistors:

R21-R27:	56 Ω
R28, R29:	100 Ω
R30:	68 Ω

Semiconductors:

D1-D10:	LED 2×5mm red
D11-D30:	LED 2×5mm yellow
D31-D100:	LED 2×5mm green

Other:



J6, J7:	goldpin strip 18mm 1×10
---------	-------------------------



Start mounting from soldering the components onto the board in order of size from smallest to largest. Photographs of the mounted kit may be helpful. To access the high-resolution images as links, download the PDF.



PDF
DOWNLOAD

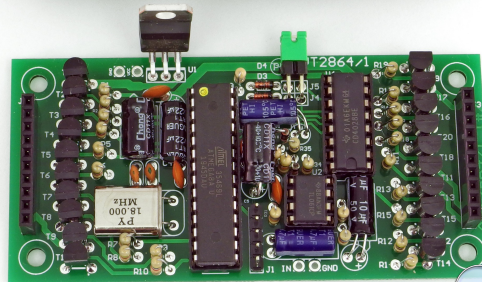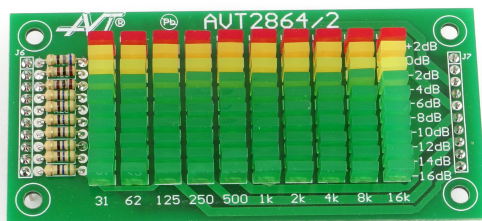

AVT SPV Sp. z o.o.

Leszczynowa 11 Street,
03-197 Warsaw, Poland
<https://sklep.avt.pl/>



This symbol means do not dispose of your product with your other household waste. Instead, you should protect human health and the environment by handing over your waste equipment to a designated collection point for the recycling of waste electrical and electronic equipment.

AVT SPV reserves the right to make changes without prior notice. Installation and connection of the appliance not in accordance with the instructions, unauthorised modification of components and any structural alterations may cause damage to the appliance and endanger persons using it. In such a case, the manufacturer and its authorised representatives shall not be liable for any damage arising directly or indirectly from the use or malfunction of the product. The self-assembly kits are intended for educational and demonstration purposes only. They are not intended for use in commercial applications. If they are used in such applications, the purchaser assumes all responsibility for ensuring compliance with all regulations